

## ENGR 120

## Homework 5

**NOTE:** Use non-engineering format for problems 1 through 4 and engineering format for problem 5 and 6. This is an individual assignment.

1. Wire a servo onto your breadboard as shown in the class notes from the previous class. Implement the program below. Write a paragraph describing how the `digitalWrite()`, `delayMicroseconds()`, and `delay()` functions work together to control servo motion. You may wire your servo to an I/O pin other than pin2 (it's your preference).

```
void setup() {
  pinMode(2, OUTPUT);
}
void loop() {
  int i;
  for (i=0; i<200; i++) {
    digitalWrite(2, HIGH);
    delayMicroseconds(1300);
    digitalWrite(2, LOW);
    delay(20);
  }
  delay(1000);
  for (i=0; i<400; i++) {
    digitalWrite(2, HIGH);
    delayMicroseconds(1700-i);
    digitalWrite(2, LOW);
    delay(20);
  }
  delay(1000);
}
```

2. Visit the following link:

<http://www.arduino.cc/en/Reference/Servo>

Enter the program below.

- Modify the program, allowing the number "1550" to range from 1300 to 1700 in increments of 50.
- Describe what happens as the argument of the `writeMicroseconds()` function is changed from 1300 to 1700.

```
#include <Servo.h>

Servo myservo1;

void setup() {
  myservo1.attach(2);    // assumes servo is on pin2
  myservo1.writeMicroseconds(1550);
}

void loop() {
}
```

3. Enter the program below.

- Describe how the program works, commenting on the `attach()` and `writeMicroseconds()` functions.
- What are the advantages of using the "Servo.h" library to control a servo compared to the method used for problem 1? **HINT:** Could you be doing something else during the 20ms of delay following the `writeMicroseconds()` command?

```

#include <Servo.h>

Servo myservo1;

void setup() {
  myservo1.attach(2);
}


void loop() {
  for (int i=0; i<=400; i++) {
    myservo1.writeMicroseconds(1300+i);
    delay(20);
  }
  delay(1000);
}

```

4. Review the PowerPoint presentation on soldering available on the class website, and complete the safety quiz. Turn the quiz in to your instructor in a separate stack of papers (don't fold the quiz in with this homework assignment).

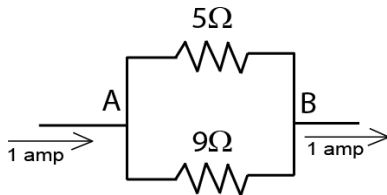5. Use the circuit below to answer the following questions:

- What is the voltage drop from point A to point B? **3.21V**
- What is the equivalent resistance of the circuit? **3.21Ω**
- What are the color codes for each of these resistors?
- What are the currents through the 5Ω and the 9Ω resistors? **0.64A through 5Ω and 0.36A through 9Ω**
- Based on your answers in part (d), is KCL satisfied at point A? Does more current pass through the 5Ω or the 9Ω resistor? Does this make sense?



6. Consider the circuit below where  $V_1 = 12V$ ,  $R_1 = 220\Omega$ ,  $R_2 = 470\Omega$ ,  $R_3 = 220\Omega$ , and  $R_4 = 100\Omega$ .

- Compute the equivalent resistance for the entire circuit. **470Ω**
- What current passes through  $R_1$ ? **26 mA**
- What is the voltage drop across  $R_1$ ? **5.62 V**
- What current passes through  $R_4$ ? **26 mA**
- What is the voltage drop across  $R_4$ ? **2.55 V**
- What is the voltage drop across  $R_2$  and  $R_3$ ? **3.83 V**
- What current passes through  $R_2$ ? **8.1 mA**
- What current passes through  $R_3$ ? **17 mA**

