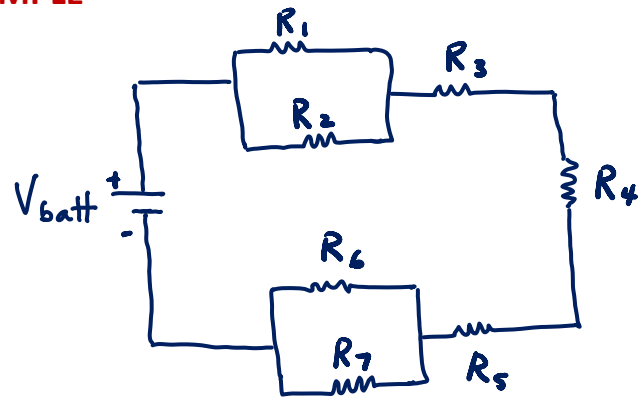


## COMBINED SERIES-PARALLEL CIRCUIT EXAMPLE

**GIVEN:** Consider the circuit shown, where

$$\begin{aligned} R_1 &= 20\Omega & R_2 &= 20\Omega & R_3 &= 5\Omega \\ R_4 &= 10\Omega & R_5 &= 15\Omega & R_6 &= 25\Omega \\ R_7 &= 100\Omega & V_{\text{batt}} &= 120\text{V} \end{aligned}$$



**REQUIRED:**


- The current leaving the battery.
- The power supplied by the battery.
- The voltage across  $R_5$ .

**SOLUTION:**

- First, combine the three resistors that are in series.

$$\begin{aligned} R_{345} &= R_3 + R_4 + R_5 = 5\Omega + 10\Omega + 15\Omega \\ R_{345} &= 30\Omega \end{aligned}$$

We can now redraw the circuit as shown.

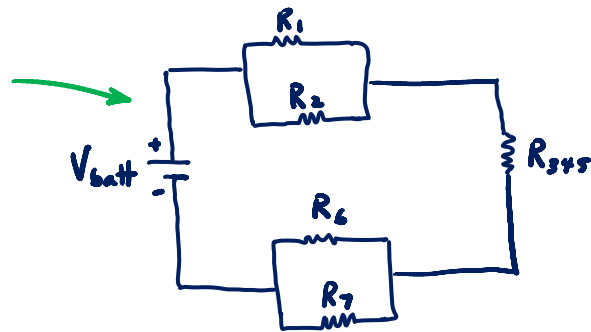


We can now combine all resistors in parallel. By inspection, we note that  $R_1$  and  $R_2$  are in parallel, and  $R_6$  and  $R_7$  are in parallel.

$$\begin{aligned} & \begin{array}{c} R_1 = 20\Omega \\ \text{---} \\ \text{---} \\ R_2 = 20\Omega \end{array} \\ R_{12} &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{1}{\frac{1}{20\Omega} + \frac{1}{20\Omega}} = \frac{1}{\frac{2}{20\Omega}} \\ R_{12} &= 10\Omega \end{aligned}$$

$$\begin{aligned} & \begin{array}{c} R_6 = 25\Omega \\ \text{---} \\ \text{---} \\ R_7 = 100\Omega \end{array} \\ R_{67} &= \frac{1}{\frac{1}{R_6} + \frac{1}{R_7}} = \frac{1}{\frac{1}{25\Omega} + \frac{1}{100\Omega}} = \frac{1}{\frac{5}{100\Omega}} \\ R_{67} &= 20\Omega \end{aligned}$$

Again, we can redraw the circuit.

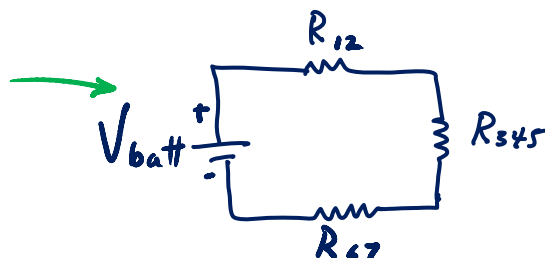


We can now find  $R_{eq}$  by combining all series resistors.

$$R_{eq} = R_{12} + R_{345} + R_{67} = 10\Omega + 50\Omega + 20\Omega$$

$$\underline{R_{eq} = 60\Omega}$$

Redrawing the circuit once more . . .

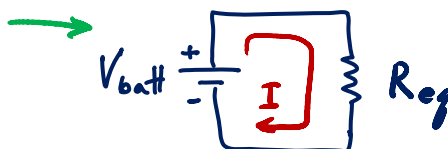

Now that we know  $R_{eq}$ , we can find the current.

$$V = IR \leftarrow \text{OHM'S LAW}$$

$$I = \frac{V_{batt}}{R_{eq}} = \frac{120V}{60\Omega}$$

$$\underline{I = 2A}$$

(b) Now that we know the current leaving the battery AND the battery voltage, we can easily compute the power.

$$P_{batt} = V_{batt} \cdot I = 120V \cdot 2A$$

$$\underline{P_{batt} = 240W}$$

(c) The voltage drop across  $R_5$  can be computed using Ohm's Law (we already know the current through  $R_5$  as well as the resistance of  $R_5$ ).

$$V_{R5} = IR_5 = 2A \cdot 15\Omega$$

$$\underline{V_{R5} = 30V}$$

#### DISCUSSION:

- The answers seem reasonable.
- The combinations of series resistors resulted in equivalent resistances which were greater than any single resistor in the combination, as expected ( $R_{345} > R_3, R_4, R_5$ )
- The combination of parallel resistors resulted in equivalent resistances less than any single resistor in the combination, as expected.
- The voltage across  $R_5$  was less than the voltage supplied by the battery, as expected.